

B.Tech II Year II Semester (R13) Supplementary Examinations May/June 2017

SWITCHING THEORY & LOGIC DESIGN

(Common to EEE and ECE)

Time: 3 hours

Max. Marks: 70

PART - A

(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- Convert the decimal number 250.5 to base 3, base 4.
 - Write and prove de-Morgan laws.
 - Implement two input EX-OR gate from 2 to 1 multiplexer.
 - What are don't cares?
 - Write the block diagram of 3-8 decoder.
 - Implement two input EX-OR gate from 2 to 1 multiplexer.
 - What are the applications of flip flops?
 - How do you build a latch using universal gates?
 - Discuss about a bidirectional shift register.
 - List the advantages of having equivalent states.

PART - B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT - I

- 2 (a) Deduce $(70.65)_8 = ()_2 = ()_{16}$
 (b) Explain 1's complement representation of signed number.

OR

- 3 (a) Deduce X from the following:
 (i) $(BA0.C)_{16} = (X)_8$. (ii) $(7562)_8 = (X)_2$. (iii) $(FFE.C)_{16} = (X)_2$.
 (b) Convert $(0011001.0101)_2$ to decimal and octal.

UNIT - II

- 4 Implement the following function with NAND gates $F(x, y, z) = \Sigma(0, 6)$.

OR

- 5 Simplify the following using Tabular method.
 $F(A, B, C, D, E) = \Sigma(0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 2, 31)$

UNIT - III

- 6 Draw the logic diagram for 4 bit binary adder-subtractor circuit and explain its operation.

OR

- 7 Implement $F(A, B, C, D) = \Sigma(0, 1, 3, 5, 6, 8, 9, 11, 12, 13)$ using 8: 1 MUX and explain its procedure.

UNIT - IV

- 8 Draw the circuit diagram of MOD-10 counter and explain the operation of it.

OR

- 9 With the aid of external logic, convert D type flip flop to a JK flip flop.

UNIT - V

- 10 (a) Write the programming table to implement BCD to Z using a PLA.
 (b) Describe briefly how PAL is used to implement logic functions.

OR

- 11 Design and implement full adder with PLA.
