

R16

Code No: 133AJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B.Tech II Year I Semester Examinations, November/December - 2018****DIGITAL LOGIC DESIGN****(Common to CSE, IT)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) Write the advantages of floating-point representation. [2]
- b) Distinguish between weighted and non-weighted codes with example. [3]
- c) What is the use of don't care combinations? [2]
- d) Implement the following function using only NOR Gates $F=a.(b+ c) + (b. c)$. [3]
- e) Define a combinational circuit , give its block diagram. [2]
- f) Write a short notes on priority encoder. [3]
- g) Differentiate between a latch and a flip flop. [2]
- h) Define Hazard. Mention various types of hazards. [3]
- i) Why programmable AND gates are used in PLA instead of a decoder. [2]
- j) Write the applications of logical micro operations. [3]

PART-B**(50 Marks)**

- 2.a) Implement AND, OR, NOR by using NAND gates only.
- b) Derive the hamming code for the sequence (101011). [5+5]

OR

- 3.a) Convert the following to the corresponding bases
 - i) $(343)_5 = ()_6$
 - ii) $(7654)_8 = ()_{10}$
- b) Explain about even and odd parity check with an example, what is the drawback. [5+5]
- 4.a) Derive the sum of minterms for $f(a,b,c,d)=a'b+ab'd+c'd$
- b) Derive and Implement Exclusive OR function involving three variables using only NAND function. [5+5]

OR

- 5.a) Obtain the simplified expression in POS (product of sums) of $F(w,x,y,z)=\pi(1,2,4,7,12,14,15)$ using K-maps.
- b) Implement the function $f(a,b,c)=\sum(1,3,4,6)$ using NOR-NOR two level gate structure. [5+5]
6. Realize a full subtractor using decoders. [10]

OR

- 7.a) Define a multiplexer? Draw a 2:1 multiplexer for the function $f(x,y,z)=\sum(0,2,3,5,7)$
- b) Write the steps involved in designing a combinational circuit. [5+5]

8. What is the drawback of JK flip flop, design a flip flop which overcomes this drawback and explain with neat diagram. [10]

OR

9.a) Draw the block diagram of asynchronous sequential circuit.

b) Analyze latch with NOR gates, derive transition, flow and state tables. [4+6]

10. Give the logic implementation of a 32×4 bit ROM using decoder of a suitable size. [10]

OR

11. What do you mean by register transfer? Explain in detail. Also discuss Three state bus buffer. [10]

---oo0oo---