

Code No: 133BJ

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year I Semester Examinations, November/December - 2017****NETWORK ANALYSIS****(Electronics and Communication Engineering)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

**PART- A****(25 Marks)**


- 1.a) Define Graph, Tree, Basic Cut set and Basic Tie set. Illustrate with an example. [2]
- b) Explain Active elements in detail. [3]
- c) Derive the relation between voltage and current in a series connected RL Circuits. [2]
- d) Draw a power triangle in series connected RLC networks. [3]
- e) Derive the relation between RMS and maximum value. [2]
- f) Define form factor and peak factor. [3]
- g) Define characteristic impedance. [2]
- h) Define image and iterative impedance. [3]
- i) Draw and explain T section network. [2]
- j) Explain about LC Filters. [3]

**PART-B****(50 Marks)**

- 2.a) What is an electric circuit? What is a magnetic circuit? Make a comparison between electric circuit and magnetic circuit.
- b) Coil 1 of a pair of coupled coils has a continuous current of 5A, and the corresponding fluxes  $\phi_{11}$  and  $\phi_{12}$  are 0.2 and 0.4 mWb respectively. If the turns are  $N_1 = 500$  and  $N_2 = 1500$ , find  $L_1$ ,  $L_2$ ,  $M$  and  $k$ . [5+5]

**OR**

- 3.a) For the network shown in below Figure 1 find  $Z_{ab}$  and  $I_o$ .

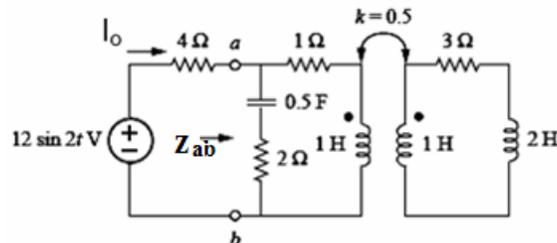**Figure: 1**

- b) Find the input impedance of the circuit shown in Figure 2. Assume that the circuit operates at  $\omega = 50$  rad/s. [5+5]

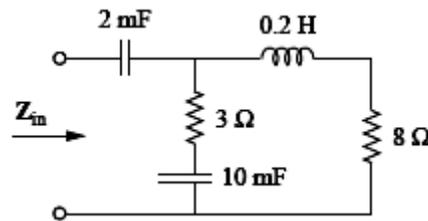


Figure: 2

- 4.a) Obtain the current locus of a fixed resistance and a variable capacitance.  
 b) Given a series RLC circuit with  $R = 10$  ohms,  $L = 1$  mH and  $C = 1$   $\mu$ F is connected across a sinusoidal source of 20 V with variable frequency. Find: i) The resonant frequency ii) Q factor of the circuit at resonant frequency iii) Half power frequencies [5+5]

OR

- 5.a) Derive and draw the response of a series RLC circuit for step input.  
 b) An impedance  $Z_1 = 10 + j10$   $\Omega$  is connected in parallel with another impedance of resistance 8.5  $\Omega$  and a variable capacitance connected in series. Find C such that the circuit is in resonance at 5 KHz. [5+5]

6. A series-connected RLC circuit has  $R = 4$  and  $L = 25$  mH:  
 a) Calculate the value of C that will produce a quality factor of 50.  
 b) Find  $\omega_1$ ,  $\omega_2$ , and B.  
 c) Determine the average power dissipated at  $\omega = \omega_0$ ,  $\omega_1$ ,  $\omega_2$ . Take  $V_m = 100$  V. [3+3+4]

OR

- 7.a) Obtain the current locus of a series circuit having a fixed resistance and a variable inductance.  
 b) Given a series RLC circuit with  $R = 100$  ohms,  $L = 0.5$  H and  $C = 40$   $\mu$ F, Calculate the resonant, lower and upper half – power frequencies. [5+5]

8. Explain clearly the terms:  
 a) Characteristic Impedance and  
 b) Image Transfer Constant. [5+5]

OR

- 9.a) Define Hybrid parameters of a Two Port network. Establish the relation between Hybrid Parameters and ABCD Parameters.  
 b) A symmetrical T-section has an inductance of 0.47H in each series arm and a 300  $\mu$ F capacitor in the shunt arm.  
 i) Find the characteristic impedance at frequencies of 50 Hz and 100 Hz.  
 ii) If the T-section is terminated in the characteristic impedance, find the ratio of load current to input current at both the frequencies. [5+5]

- 10.a) What is a high pass filter? In what respects it is different from a low pass filter?  
b) Derive the equations to find the inductances and capacitances of a constant K high pass filter. [5+5]

**OR**

- 11.a) What is an LC immittance function? State the properties of such functions.  
b) Design a constant 'K' T-section low pass filter having cutoff frequency of 2 kHz and nominal characteristic impedance of 600 ohms. [5+5]

---oo0oo---