

Code No: 126VN

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B.Tech III Year II Semester Examinations, December - 2018****VLSI DESIGN****(Common to ECE, ETM)****Time: 3 hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART - A**(25 Marks)**

- 1.a) Write about the Pass transistor. [2]
- b) Distinguish between Enhancement and Depletion mode transistor action in N-MOS. [3]
- c) Write about contacts and vias in layout design. [2]
- d) Write about the 1.2 μm double metal single poly CMOS rules. [3]
- e) Mention the different forms of Time delays in gate level circuits. [2]
- f) Explain about Switch logic and its usage. [3]
- g) Distinguish a synchronous and an asynchronous counters. [2]
- h) Write a note on Content Addressable Memory. [3]
- i) What is the need for testing of IC? [2]
- j) What are the different chip-level Test Techniques? [3]

PART - B**(50 Marks)**

- 2.a) Explain the CMOS fabrication process in p-well using suitable diagrams.
- b) Discuss the effect of threshold voltage on MOSFET current Equations. [5+5]

OR

- 3.a) Discuss the MOS transistor Characteristics in Depletion and enhancement modes.
 - b) Write about Alternative forms of pull-up and describe about the NMOS pull-ups. [5+5]
4. Write about the stick diagrams and design a stick diagram for two input N-MOS NAND and NOR gates. [10]

OR

- 5.a) Distinguish between the Lambda-base rules and Double metal MOS process rules.
 - b) Draw the neat layout diagrams for NMOS shift register cell. [5+5]
- 6.a) Explain the formal estimation of CMOS inverter delay rise-time estimation and Fall-time estimation.
- b) Write a note on the Wiring capacitance in detail. [5+5]

OR

- 7.a) Write about the different Alternate gate circuits in detail.
- b) Discuss about the Choice of layers for the gate level design. [5+5]

- 8.a) Explain the working principle of Ripple carry adder using Transmission Gates.
b) Explain about the configurations and applications of SRAM and DRAM cells. [5+5]

OR

- 9.a) Explain the Principle and structure of Serial-Parallel multiplier.
b) Describe the design procedure for design of a asynchronous counter. [5+5]

- 10.a) Design a PAL to realize a full Adder circuit.
b) Explain the detailed Architecture of CPLD and its Implementations. [5+5]

OR

11. Write a short note on the following:
a) CMOS Testing
b) Strategies for testing. [5+5]

---ooOoo---