

**DIGITAL LOGIC DESIGN**

(Common to Computer Science and Engineering and  
Information Technology)

**Time: 3 Hours****Max. Marks: 60****Note:** All Questions from **PART-A** are to be answered at one place.Answer any **FOUR** questions from **PART-B**. All Questions carry equal Marks.**PART-A****6 × 2 = 12M**

1. Distinguish between 1's complement and 2's complement numbers.
2. Explain minimal SOP and POS forms?
3. Draw the truth table of Full Adder?
4. Realize 1-to-4 demultiplexer using 1-to-2 demultiplexers.
5. Realize a T Flip Flop using D Flip Flop?
6. List the applications of registers.

**PART-B****4 × 12 = 48M**

1. a) Solve for X. (6M)  
i)  $(789)_{16} + (478)_8 = (X)_4$       ii)  $(4085.025)_{10} = (X)_{15}$   
b) Convert the following numbers. (6M)  
i)  $(1984)_{10}$  to base 8      ii)  $(53.1575)_{10}$  to base 2      iii)  $(3A6)_{16}$  to decimal
2. a) Realize all basic logic gates using universal gates. (6M)  
b) Simplify the following Boolean functions using Karnaugh maps to a minimum number of terms. (6M)  
i)  $F(A,B,C,D) = \sum m(0,1,2,4,6,9,10)$       ii)  $F(a,b,c) = \sum m(1,2,5,7) + d(0)$
3. a) Draw the diagram for a 4 bit adder/subtractor circuit and explain its operation. (6M)  
b) Construct a full adder using XOR and NAND gates only. (6M)
4. a) Implement Full Adder circuit using PAL? (6M)  
b) Realize a 4-bit BCD to Gray Code converter using PLA? (6M)
5. a) Explain any 2 Flip Flops using Truth tables and Excitation Tables. (6M)  
b) Design a Synchronous Decade Counter using D Flip Flop? (6M)
6. a) Draw the diagram of universal shift register and explain in detail. (6M)  
b) Draw and explain in detail about 4-bit Johnson Counter. (6M)

\*\*\*\*\*