

B.Tech II Year II Semester (R15) Regular Examinations May/June 2017

ELECTRONIC CIRCUIT ANALYSIS

(Common to ECE and EIE)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- (a) Identify different types of feedback available.
 - (b) Write the condition for generating oscillations.
 - (c) Draw the hybrid equivalent model of CE amplifier.
 - (d) Mention four h-parameters of CE amplifier.
 - (e) Identify different types of coupling used in amplifiers.
 - (f) Write the advantages of multistage amplifier.
 - (g) Draw the circuit of transformer couple power amplifier.
 - (h) Mention the efficiency of class-B power amplifier.
 - (i) List out applications of tuned amplifiers.
 - (j) Draw the circuit diagram of matched capacitive coupled amplifier.

PART – B
(Answer all five units, 5 X 10 = 50 Marks)**UNIT – I**

- 2 Draw the circuit of voltage shunt feedback amplifier and derive the expressions for A_v , R_i , R_o .
- OR**
- 3 (a) Write the advantages and disadvantages of positive and negative feedback.
(b) Derive the expression for frequency of Wein bridge oscillator.

UNIT – II

- 4 Explain about Hybrid π capacitance and also briefly discuss miller's theorem.
- OR**
- 5 Derive the expressions for hybrid π model parameters g_m , g_{ce} , r_{ce} .

UNIT – III

- 6 Explain different types of coupling. When two identical stages are cascaded, obtain voltage gain, current gain and power gain.
- OR**
- 7 Draw and explain the circuit of cascade amplifier and mention the advantages.

UNIT – IV

- 8 Draw and explain class-B push pull amplifier.
- OR**
- 9 (a) Compare various types of power amplifier.
(b) Write about importance of heat sink in power amplifiers.

UNIT – V

- 10 Derive the expression for Q factor of double tuned amplifier.
- OR**
- 11 Write the effect of cascading single tuned amplifier on bandwidth.
