

Code No: 114CV

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY, HYDERABAD

B.Tech II Year II Semester Examinations, May - 2015

ELECTRONIC CIRCUIT ANALYSIS

(Common to ECE, EIE)

Time: 3 Hours

Max. Marks: 75

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.


Each question carries 10 marks and may have a, b, c as sub questions.

**PART - A****(25 Marks)**

- 1.a) State and explain Miller's theorem. [2M]
- b) How are amplifiers classified based on their duration of transistor conduction? [3M]
- c) Write the significance of Gain- Band width product of an amplifier. [2M]
- d) List out the elements of a CE amplifier which influence its lower cut-off frequency. [3M]
- e) What is the effect of negative feedback in current series type feedback amplifier? [2M]
- f) State Barkhausen criteria for oscillations. [3M]
- g) List the merits and demerits of push-pull configuration in power amplifiers. [2M]
- h) What are the heat sinks? Why are they needed? [3M]
- i) Define Q-Factor of a tuned amplifier. What is its ideal value? [2M]
- j) Differentiate between synchronous tuning and staggered tuning of cascaded tuned amplifiers. [3M]

**PART - B****(50 Marks)**

- 2.a) Draw the circuit diagram of Darlington amplifier and derive the expressions for overall current gain and overall input impedance.
- b) Compute the voltage gain, current gain and input impedance for the amplifier circuit shown in figure 1. Assume  $h_{ie}=1.1k\Omega$  and  $h_{fe}=60$ . Also assume that the effects of  $h_{re}$  and  $h_{oe}$  are negligible. [5+5]

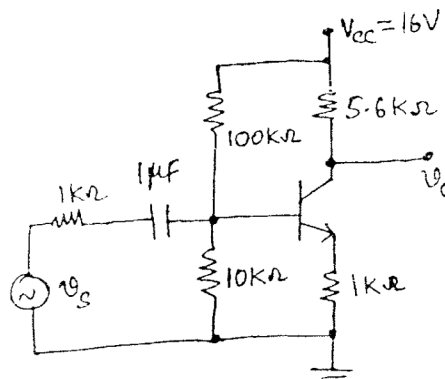

**Figure: 1**  
**OR**

- 3.a) Draw the circuit diagram, equivalent circuit of an emitter follower amplifier and derive the expression for its voltage gain, current gain and input impedance.
- b) For the CE-CC amplifier cascade shown in figure 2, obtain overall voltage gain. Assume typical values of h-parameters. [5+5]

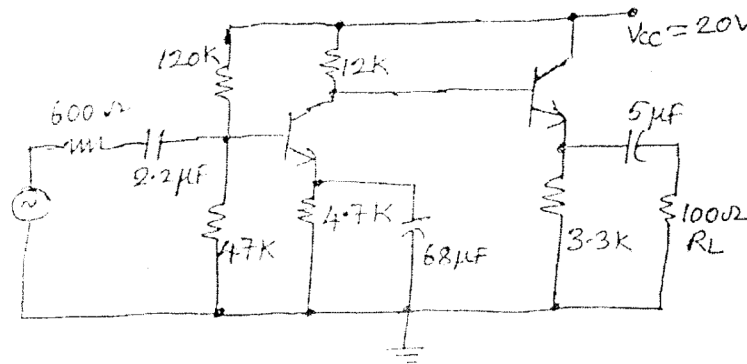


Figure: 2

- 4.a) Discuss the effect of coupling and bypass capacitors on the frequency response of a CE amplifier.
- b) Draw the circuit diagram of a MOS common source amplifier and explain its operation. Derive the expressions for voltage and current gains based on its equivalent circuit. [4+6]

OR

- 5.a) Draw the hybrid  $-\pi$  equivalent circuit of a BJT in CE configuration. Obtain its conductance of  $g_{ce}$  and  $g_{be}$  in terms of its low frequency h- parameters.
- b) Draw the MOS small signal model, circuit diagram and equivalent circuit of MOS CS amplifier. [5+5]

- 6.a) Establish the conditions for oscillations in a BJT based RC phase shift oscillator.
- b) Draw the block schematics of voltage series and current shunt feedback amplifiers and explain the operation. [5+5]

OR

- 7.a) Establish the gain and phase conditions for oscillations in a colpitts oscillator.
- b) Calculate the closed loop gain  $A_{CL}$  for a voltage series negative feedback amplifier if its open loop voltage gain  $A_v$  and feedback factor  $\beta$  are listed as  $10^5$  and 0.01 respectively. Calculate  $A_{CL}$  if  $A_v$  increases by 40%. [6+4]

- 8.a) Show that the maximum conversion efficiency in a class B power amplifier is 78.5%.
- b) Draw the circuit diagram of a transformer coupled class A power amplifier and explain its operation. [5+5]

OR

- 9.a) Draw the circuit diagram of a class B complementary- symmetry power amplifier and explain its operation. Obtain the expressions for conversion efficiency and collector circuit efficiency.
- b) Explain how temperature related problems are handled in power amplifiers. [6+4]

10. Draw the circuit diagram, equivalent circuit of a capacitively coupled single tuned amplifier and derive the expression for Q- Factor, voltage gain and band width.

[10]

**OR**

- 11.a) Discuss about the need and procedure for ensuring stability in a tuned amplifier.  
b) An RLC circuit used as load in a tuned amplifier has  $Z_{\max} = 70\text{k}\Omega$  at  $f=100\text{kHz}$ . The Q of the tuned circuit is 100. Compute the frequency at which the impedance becomes  $50\text{k}\Omega$ .

[5+5]

----ooOoo----