

Code No: 113BU

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, February/March - 2016

SWITCHING THEORY AND LOGIC DESIGN

(Common to ECE, EIE, ETM)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**[25 Marks]**

1. a) Determine the possible base of the numbers in the operation $302/20=12.1$. [2]
- b) Reduce the expression $A'B(D'+C'D)+B(A+A'CD)$ to one literal. [3]
- c) What are static hazards ? [2]
- d) Construct full adder using decoder. [3]
- e) What is the difference between characteristic table and excitation table? [2]
- f) Show the characteristic equation for the true output of JK flip-flop is $Q(t+1)=JQ'+K'Q$ [3]
- g) How many bit counter is needed to provide a clock with cycle time of 50ns if the clock generator produces pulses at a frequency of 80 MHz? [2]
- h) Compare Synchronous and Asynchronous counters. [3]
- i) What are compatible states? [2]
- j) Explain the difference between ASM and conventional flow chart with respect to timing. [3]

PART- B**[50 Marks]**

- 2.a) State De-Morgan laws.
 - b) Perform the following arithmetic operations in binary using signed 2's complement representation for negative numbers (i) $(+62) + (-23)$ (ii) $(-62) - (-23)$.
 - c) Encode the information character 01101110101 according to the 15 bit Hamming. [2+4+4]
- OR**
- 3.a) Obtain the 1's and 2's complement of the binary numbers 10000000 and 0000001.
 - b) Show that a positive logic NAND gate is a negative logic NOR gate and vice versa.
 - c) Obtain the truth-table of the function $(xy+z)(y+xz)$ and express the function in sum of min terms and product of max terms. [2+4+4]
- 4.a) For the function $F(w,x,y,z)=\sum(1,2,3,5,13) + \sum\phi(6,7,8,9,11,15)$, find the minimal sum of products and product of sums expression.
 - b) Implement the function $F(A,B,C,D)=\sum(0,1,3,4,6,8,15)$ using 4x1 MUX. [5+5]
- OR**
- 5.a) Design a 3-input majority circuit using Multiplexer whose output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise.
 - b) Find the min terms of the function $wxy+x'z'+w'xz$ by plotting the function in a map. [5+5]
- 6.a) Compare Sequential and Combinational circuits.
 - b) Design a JK flip-flop using D flipflop, 2-to-1 line MUX and inverter. [4+6]

- 7.a) What is the difference between a latch and flip-flop?
 b) Explain the positive edge triggered D flip-flop with asynchronous reset. [4+6]
- 8.a) A sequential circuit with two D flip-flops A and B, two inputs x and y; and one output z is specified by $A(t+1)=x'y+xA$, $B(t+1)=x'B+xA$, $z=B$. Draw the logic diagram and list the state table. Draw the state diagram.
 b) What is a universal shift register? [8+2]

OR

- 9.a) Design a counter using T flip-flops with repeated sequence 0,1,3,7,6,4.
 b) Show that a Johnson counter with n flip-flops produces a sequence of $2n$ states. [5+5]

10.a) Draw the multilevel NAND circuit for expression $F = (AB' + CD')E + BC(A + B)$

b) Reduce the given expression to a minimum number of literals:

i) $\overline{(BC' + A'D)} \overline{(AB' + CD')}$

ii) $AB' + CD\overline{(A + B)}$. [5+5]

OR

11.a) Find the equivalence partition and corresponding reduced machine in standard form.

| PS | NS,Z | |
|----|------|-----|
| | x=0 | x=1 |
| A | F,0 | B,1 |
| B | G,0 | A,1 |
| C | B,0 | C,1 |
| D | C,0 | B,1 |
| E | D,0 | A,1 |
| F | E,1 | F,1 |
| G | E,1 | G,1 |

b) Explain the control implementation using MUX. [6+4]

--oo0oo--