

H.T.No.

--	--	--	--	--	--	--	--	--	--

Code No: EC1502

GEC-R14

II B. Tech I Semester Supplementary Examinations, May 2016

SEMICONDUCTOR DEVICES AND CIRCUITS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 60

Note: All Questions from **PART-A** are to be answered at one place.

Answer any **FOUR** questions from **PART-B**. All Questions carry equal Marks.

PART-A

6 × 2 = 12M

1. Define Static resistance, dynamic resistance of a PN diode.
2. Draw the diagram associated in converting AC input to pure DC output & explain the blocks.
3. The transistor has $I_E = 10\text{mA}$ & $\alpha = 0.98$. Determine the value of I_B & I_C .
4. What is thermal runaway? What is the condition for thermal stability?
5. Compare JFET with MOSFET.
6. Justify the validity of approximate hybrid model applicable in low frequency region.

PART-B

4 × 12 = 48M

1. a) Explain V-I characteristics of a PN junction diode. (6M)
b) Explain the following (6M)
 - i) Open circuited PN junction.
 - ii) Varactor Diode.
2. a) Derive the expression for the ripple factor in a full wave rectifier using induction filter. (6M)
b) A zener diode shunt regulator circuit is to be designed to maintain a constant load current of 400mA and voltage of 40V. The input voltage is $90 \pm 5\text{V}$. The zener diode voltage is 40V and its dynamic resistance is 2.5Ω . find the following quantities for the regulator: a) the series dropping resistance, b) zener power dissipation and c) load resistance. Assume the zener current to be 10% of load current. (6M)
3. a) Explain the V-I characteristics of UJT and also define intrinsic stand-off ratio. (6M)
b) Explain the two types of break down Mechanisms in detail? (6M)

4. a) A germanium transistor having $\beta=100$ and $V_{BE}=0.2V$ is used in a fixed bias amplifier circuit where $V_{CC}=16 V$, $R_C=5k\Omega$, $R_B = 790k\Omega$. Determine its operating point. (6M)
- b) Draw a voltage divider bias circuit and derive an expression for its stability factor. (6M)
5. a) Explain the construction and operation of N channel JFET with neat diagrams. (6M)
- b) A FET has a driven current of 4mA. If $I_{DSS} = 8mA$ and $V_{GS (off)} = -6V$. Find the values of V_{GS} & V_P . (6M)
6. a) Determine A_I , A_V , R_I and R_O for a common collector circuit. (6M)
- b) Explain the common source FET amplifier using small signal model. (6M)
